

$$1) \frac{u_{q1}}{R_1} + \frac{u_{q3}}{R_3} = u_{10} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - u_{20} \frac{1}{R_3}$$

$$-\frac{u_{q3}}{R_3} + \frac{u_{q4}}{R_4} = -u_{10} \frac{1}{R_3} + u_{20} \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5+R_6} \right)$$

$$I_1 = \frac{u_{q1} - u_{10}}{R_1} \quad I_2 = \frac{u_{10}}{R_2} \quad I_3 = \frac{u_{10} - u_{20} - u_{q3}}{R_3} \quad I_4 = \frac{u_{q4} - u_{20}}{R_4}$$

$$I_5 = \frac{u_{20}}{R_5 + R_6}$$

$$2) \quad \boxed{t < 0} \quad \boxed{t = 0} \quad \boxed{t \rightarrow \infty}$$


$$u_C = u_q$$

$$u_{R2} = u_C = u_q = 24V$$

$$i_C = 0$$

$$i_C = -i_{R2} = -\frac{u_q}{R_2} = -0,16A$$
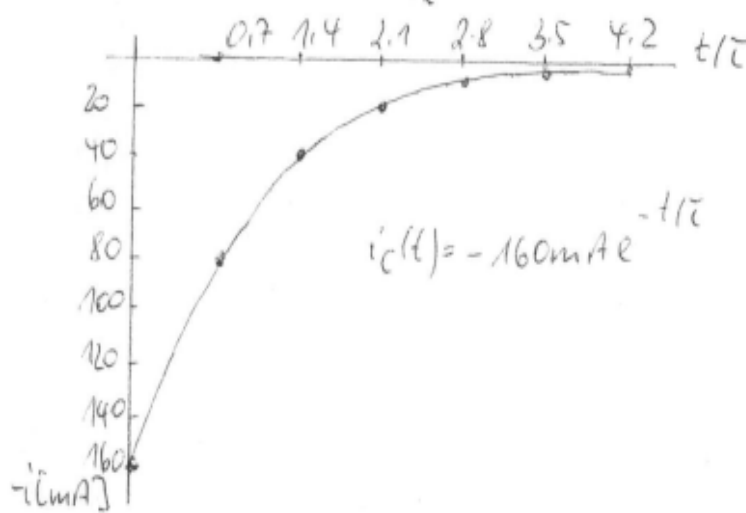
$$u_{R2} = u_C = \frac{u_q \cdot R_2}{R_1 + R_2} = 14,4V$$



$$\tau = C(R_1 || R_2) = 132 \mu s$$

$$3) \quad B_k = \frac{B_5}{1.6} = 0,94T \rightarrow \text{Kennlinie } H_k = 2A/cm$$

$$\Theta = \omega I = \oint H \cdot d\vec{l} = H_k l_e + H_0 \cdot \delta = H_k l_k + \frac{B_5}{\mu_0} \cdot \delta$$

$$= 24A + 127,3A = 151,3A$$

$$\underline{I} = \frac{\Theta}{\mu_0} = \underline{1,51A}$$

$$4) \quad \hat{I} = 1,2A e^{-j60^\circ}$$

$$\hat{I}_R = \hat{I} \cdot \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1,2A e^{-j60^\circ} \cdot 7\Omega e^{-j90^\circ}}{5\Omega - j7\Omega}$$

$$\hat{I}_R = \frac{8,4Ve^{-j150^\circ}}{8,6\Omega e^{-j54,46^\circ}} = 0,98A e^{-j95,54^\circ}$$

$$i_R = 0,98A \sin(\omega t - 95,54^\circ)$$